










# Basic Passive Components

	<u>Fixed</u>	<u>Variable</u>	
▶ Resistor (Ohms)			R
▶ Capacitor (Farads)			C
▶ Inductor (Henries)			L
▶ Transformer			T
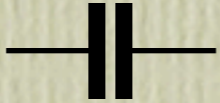
# Things to know!

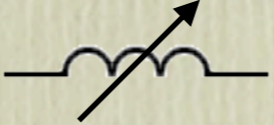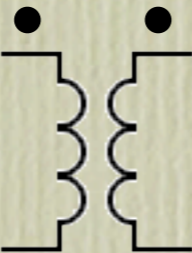---

- ▶ Voltage is designated by  $V$  (Volts) (or sometimes  $E$ )
- ▶ Current is designated by  $I$  (Amps)
- ▶ Power is designated by  $P$  (Watts)
  
- ▶ Your powers of 10: Pico, nano, micro, milli, kilo, mega, giga
- ▶ High school algebra for series and parallel circuits
- ▶ Very basic knowledge of complex numbers for  $X_C$  and  $X_L$

# Powers of Ten - Steps of 1000

Giga (G)	$10^9$	1,000,000,000
Mega (M)	$10^6$	1,000,000
kilo (k)	$10^3$	1,000
	$10^0$	1
milli (m)	$10^{-3}$	0.001
micro ( $\mu$ )	$10^{-6}$	0.0000001
nano (n)	$10^{-9}$	0.0000000001
pico (p)	$10^{-12}$	0.0000000000001

# Resistor




## Characteristics:

- Resists the flow of current
  - In theory, equal resistance to AC or DC (No reactance)
- Doesn't store energy
  - Power is dissipated as heat
- Voltage and current are in phase
- Non-polarized
- Metal Film, Wirewound, Carbon
- Variable: Rheostat (2 pins), Potentiometer (3 pins)
- Large range of values –  $m\Omega$  to  $G\Omega$
- Large range of power – mW to KW
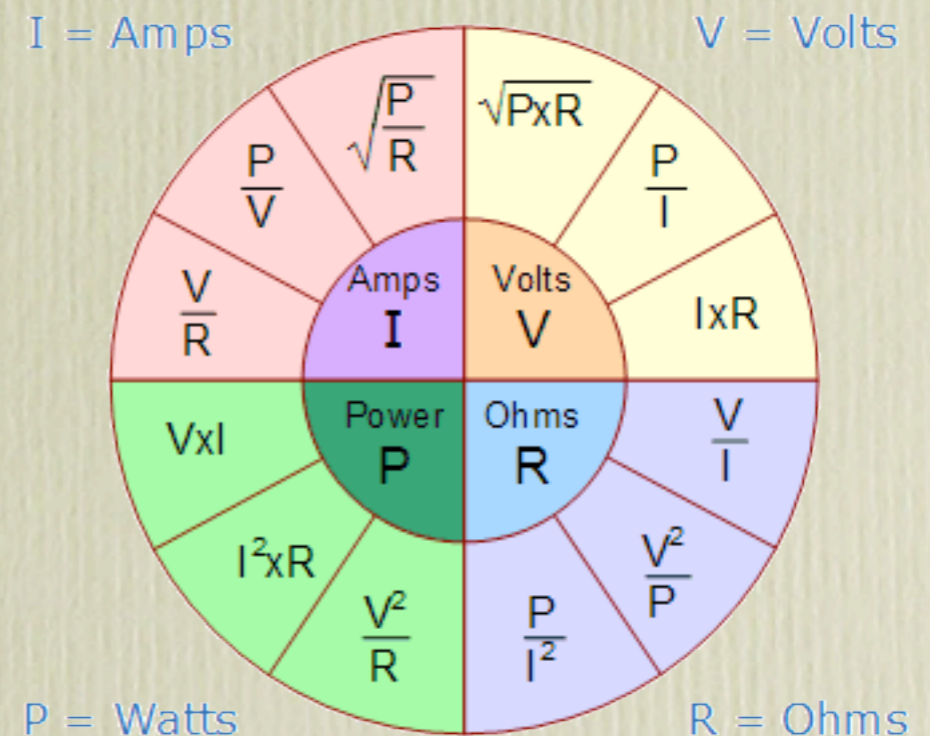
## Formulas:

- $V = I * R$  (Ohm's Law)
  - Voltage = Current \* Resistance
- $P = V * I$  or  $P = I^2 * R$ 
  - Power = Voltage \* Current



# Resistor



# Test Questions

---

T5D06: What is the resistance of a circuit that draws 4 amperes from a 12-volt source?

- A) 3 ohms
- B) 16 ohms
- C) 48 ohms
- D) 8 Ohms

•  $R = V / I \rightarrow R = 12 / 4 = 3 \text{ Ohms (A)}$

T5D07: What is the current flow in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

- A) 9600 amperes
- B) 200 amperes
- C) 0.667 amperes
- D) 1.5 amperes

•  $I = V / R \rightarrow I = 120 / 80 = 1.5 \text{ Amperes (D)}$


T5D10: What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

- A) 1.0 volt
- B) 0.25 volts
- C) 2.5 volts
- D) 1.5 volts

•  $V = I * R \rightarrow V = 0.5 * 2 = 1.0 \text{ Volt (A)}$


# Series / Parallel Resistors

## Series:

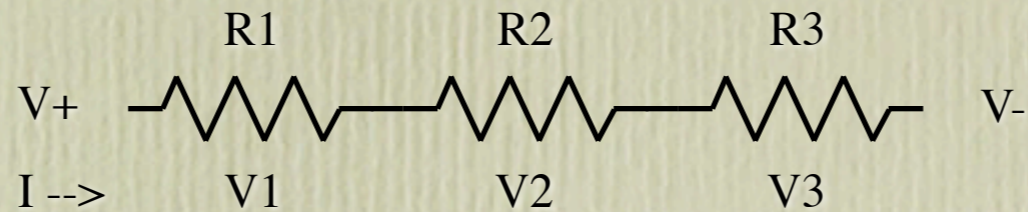

- $R_t = R_1 + R_2 + \dots$
- Always LARGER than the largest value
- Current is the same through all resistors
- Voltage across each resistor is dependent on the individual resistor values

## Parallel:

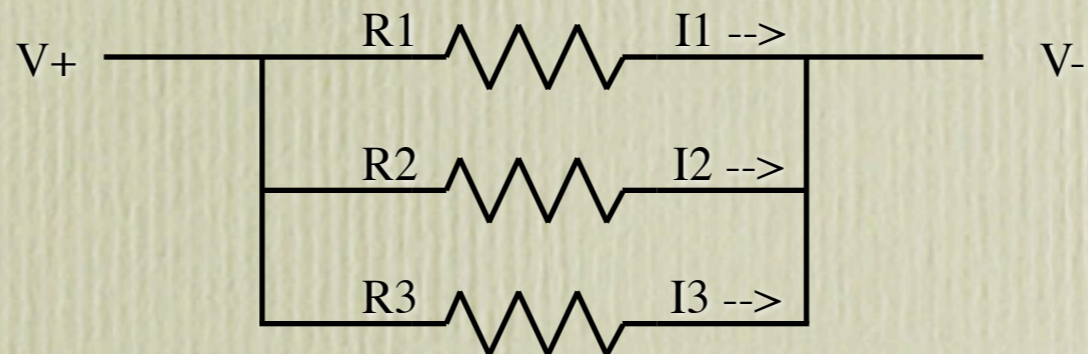

- $R_t = 1 / (1/R_1 + 1/R_2 + \dots)$
- Always SMALLER than the smallest value
- For two resistors,  $R_t = (R_1 * R_2) / (R_1 + R_2)$
- Voltage is the same across all resistors
- Current through each resistor is dependent on the individual resistor values



# Test Questions

---

G5C05: If three equal value resistors in series produce 450 ohms, what is the value of each resistor?

- A) ~~1500 ohms~~
- B) 90 ohms
- C) 150 ohms
- D) 175 ohms

•  $R = R_t/3 = 450 / 3 = 150 \text{ Ohms (C)}$

G5C15: What is the total resistance of a 10 ohm, a 20 ohm, and a 50 ohm resistor connected in parallel?

- A) 5.9 ohms
- B) 0.17 ohms
- C) ~~10000 ohms~~
- D) ~~80 ohms~~

•  $R_{t1} = (R1 * R2) / (R1 + R2) \rightarrow R_{t1} = (10 * 20) / (10 + 20) = 200 / 30 = 6.667 \text{ Ohms}$

$R_t = (R_{t1} * R3) / (R_{t1} + R3) = (6.667 * 50) / (6.667 + 50) = 333.333 / 56.667 = 5.88 \text{ Ohms (A)}$

- OR -

•  $R_t = 1 / (1/R1 + 1/R2 + 1/R3) = 1 / (0.1 + 0.05 + 0.02) = 1 / 0.17 = 5.88 \text{ Ohms (A)}$

- OR - Use currents, Assume 50V to make the math easy


•  $[I(50\Omega) = 1A] + [I(20\Omega) = 2.5A] + [I(10\Omega) = 5A] \rightarrow I_t = 8.5A$

$R_t = V/I = 50 / 8.5 = 5.88 \text{ Ohms (A)}$

# Uses


- Convert Current to Voltage

$$V = I * R$$

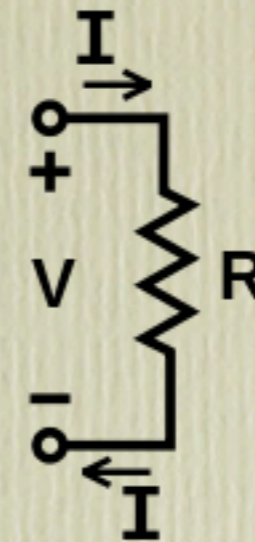

- Gain Setting

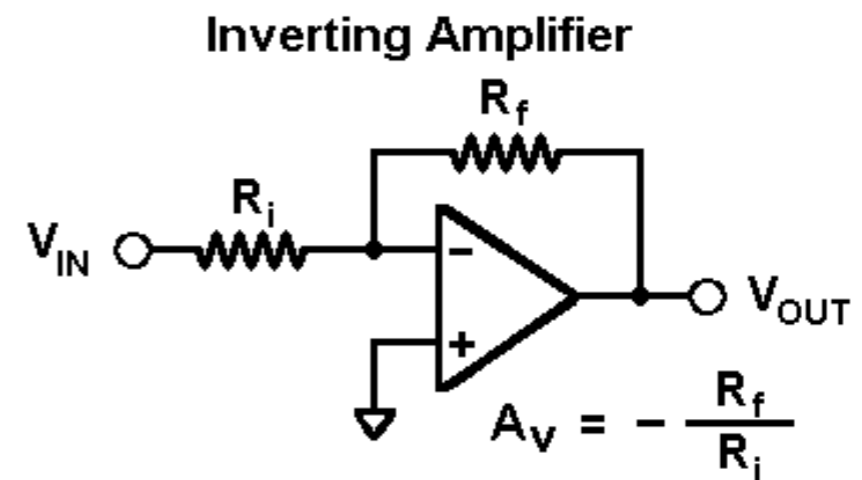
Ratio of resistance values determines amplifier gain



# Uses

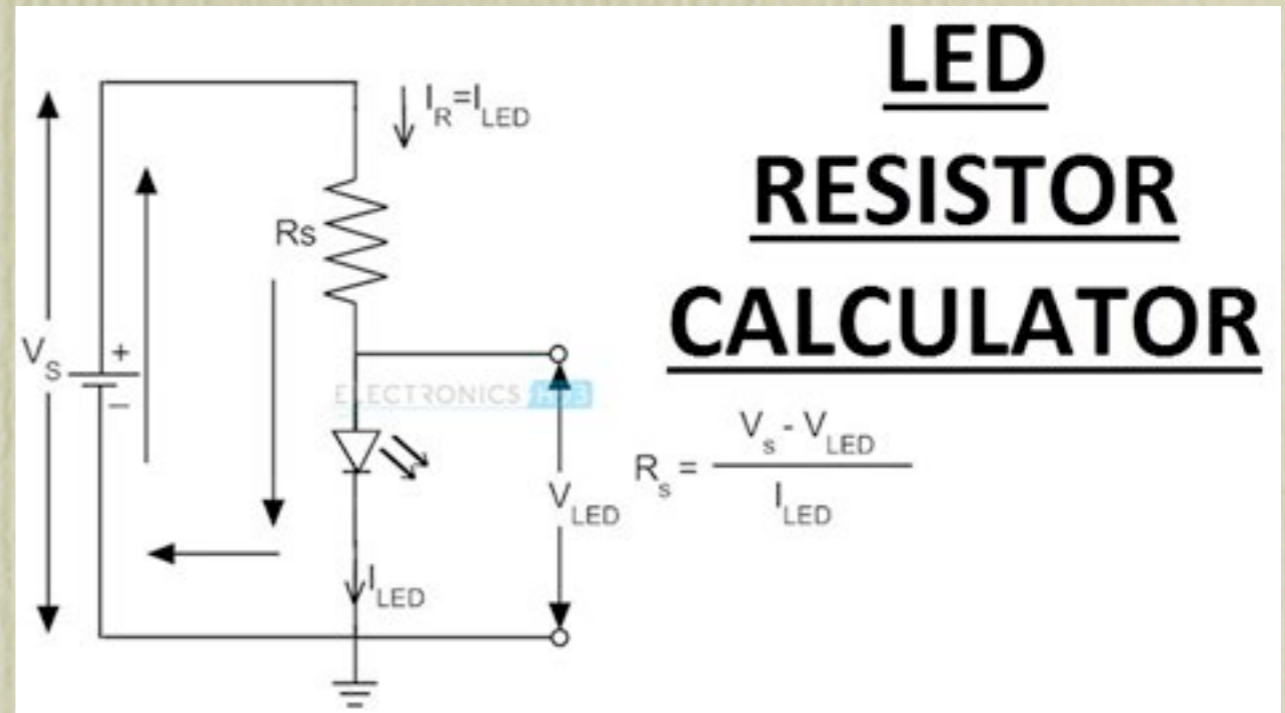
## ► Limit circuit current

Drop excess voltage to prevent LED burn out



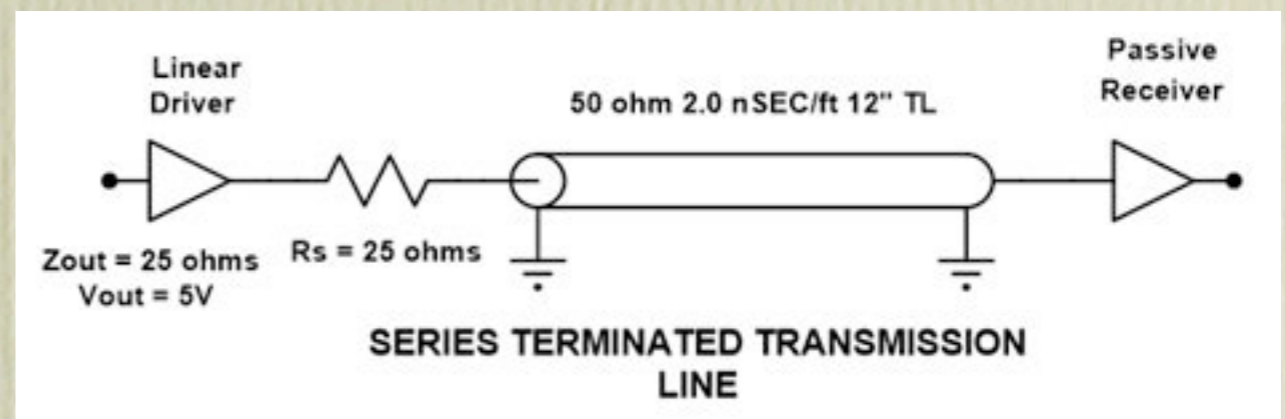
## ► Match impedance


Very inefficient at high power, but used a lot on high speed PCB traces





# Impedance Plots

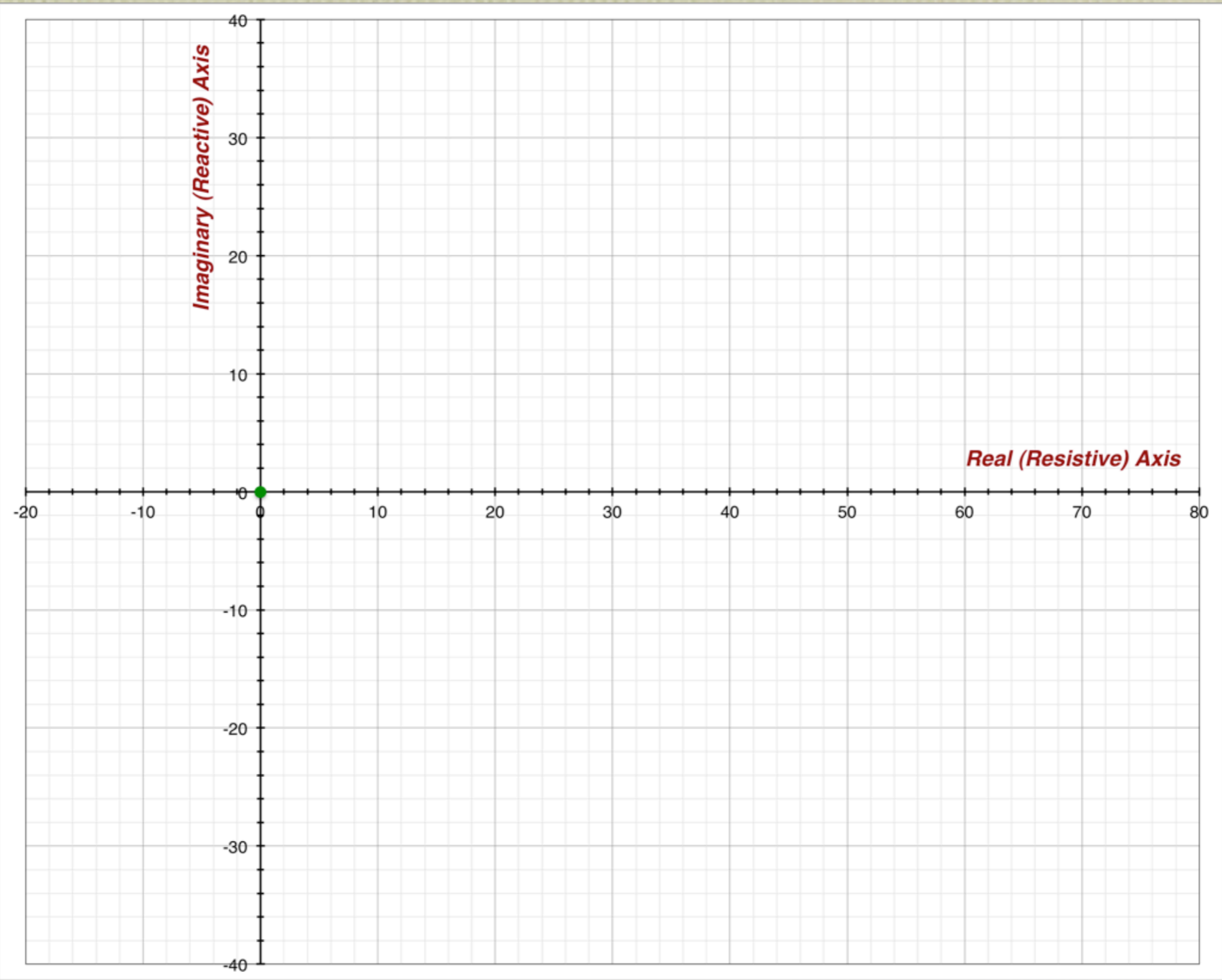


# Impedance Plot

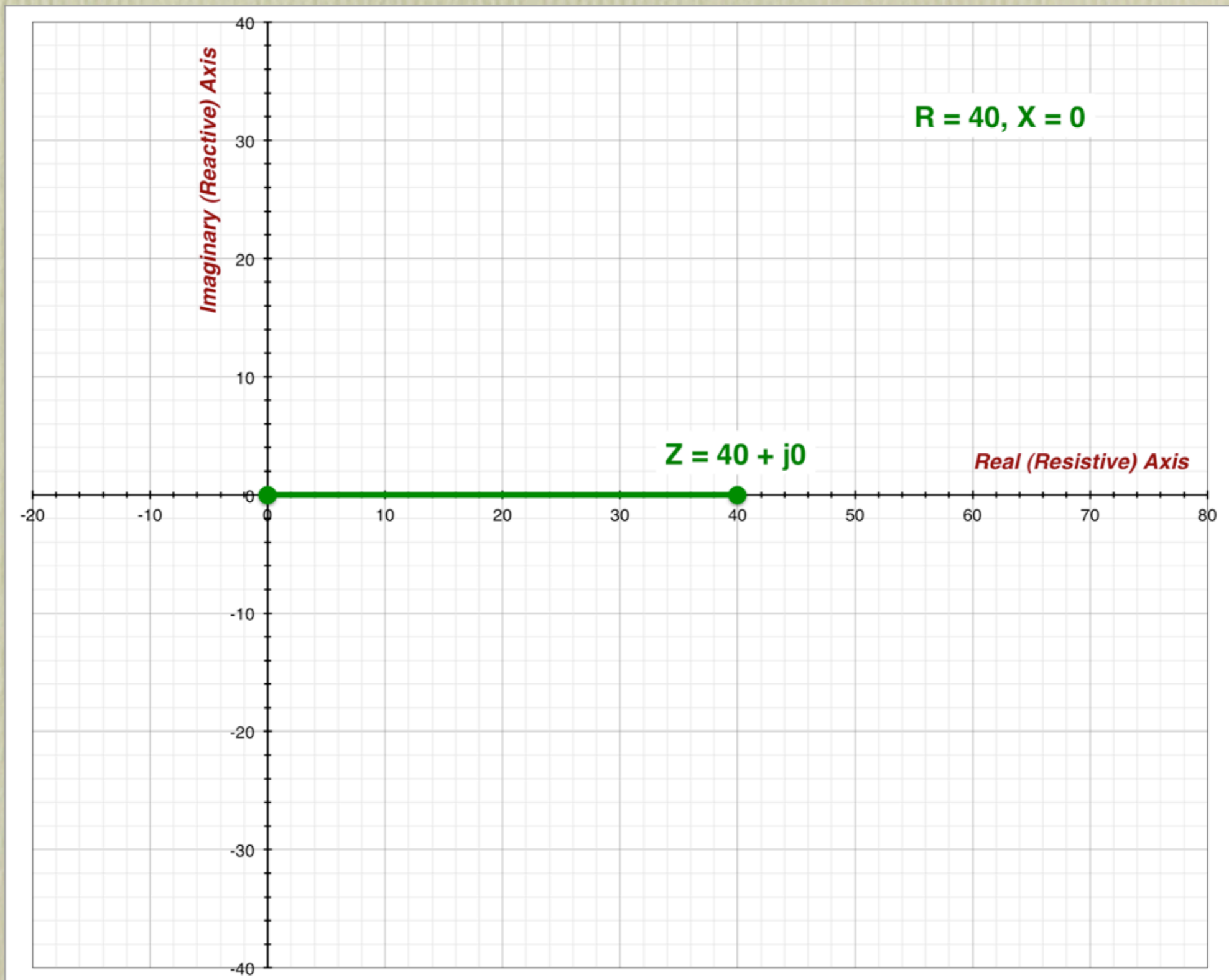

# Sine waves and phase angles

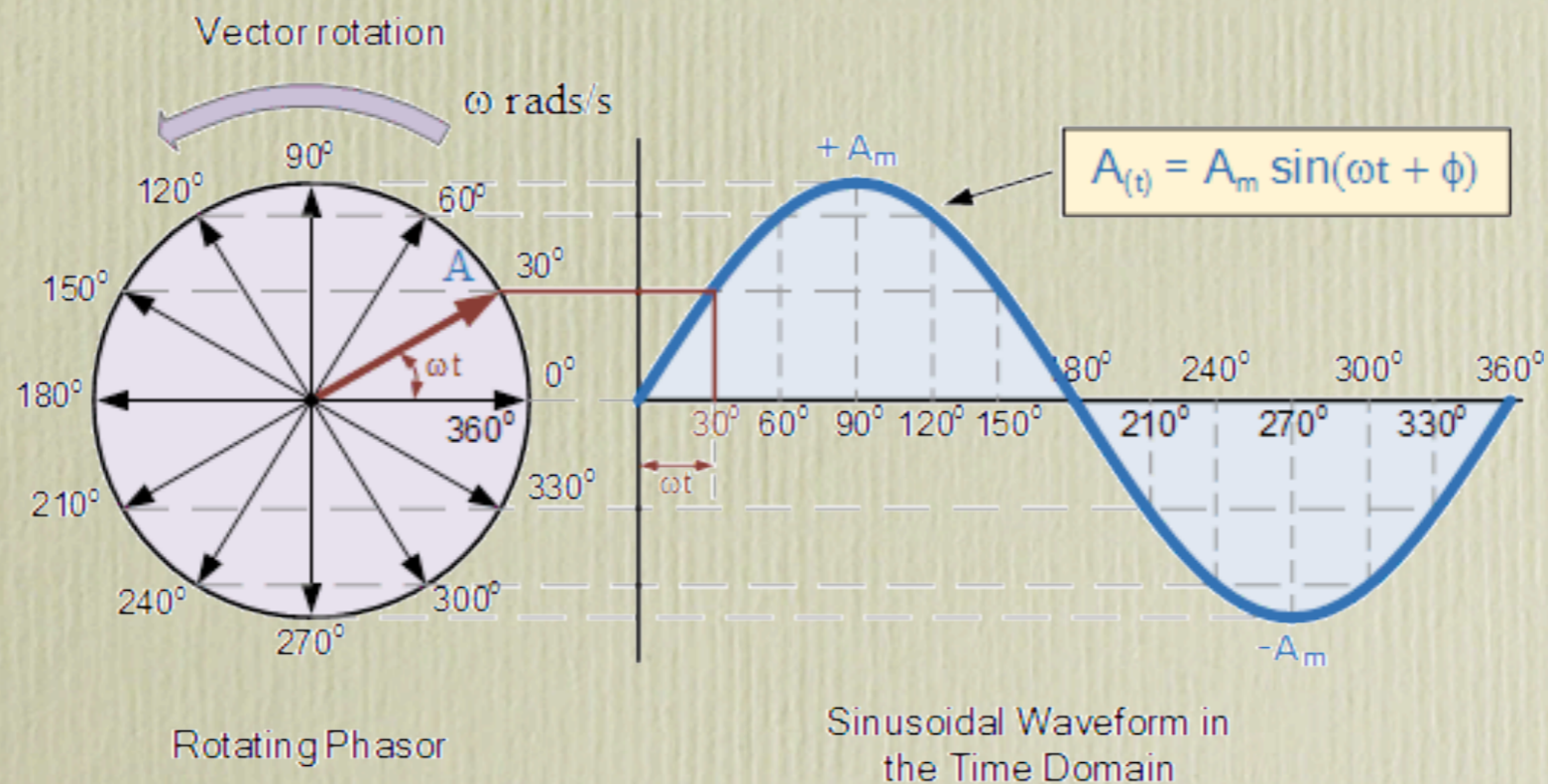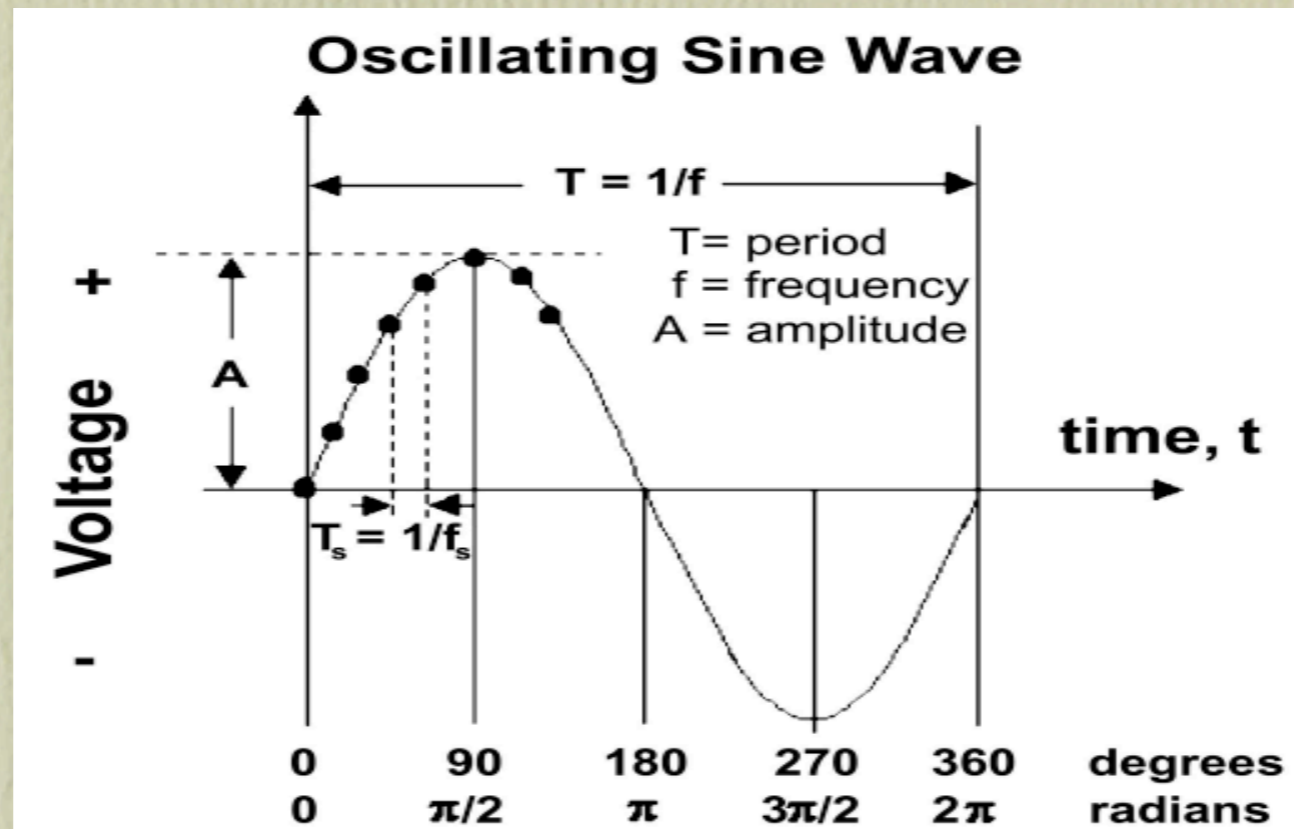

# Capacitor

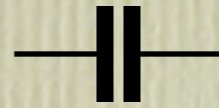

## Characteristics:

- Resists a CHANGE in voltage
- Stores energy in an electric field
  - Ideally any input energy is returned to the source
- Non-polarized: Air, Ceramic, Film, Mica
- Polarized: Electrolytic (Aluminum, Tantalum)
- Variable: Generally air (2 pins)
- Usually from pF to  $\mu\text{F}$
- Passes AC, Blocks DC
- Current through the capacitor leads the voltage by  $90^\circ$  -- ELI the ICE man
- Capacitive reactance has a negative phase angle ( $-jX$ )

## Formulas:

- $X_C = 1 / (2\pi fC)$ ; Reactance decreases with increase in frequency or capacitance
- $I = C \, dv/dt$ 
  - Current = Capacitance \* Change in voltage with respect to time


# Capacitor






# Series / Parallel Capacitors

## Series:

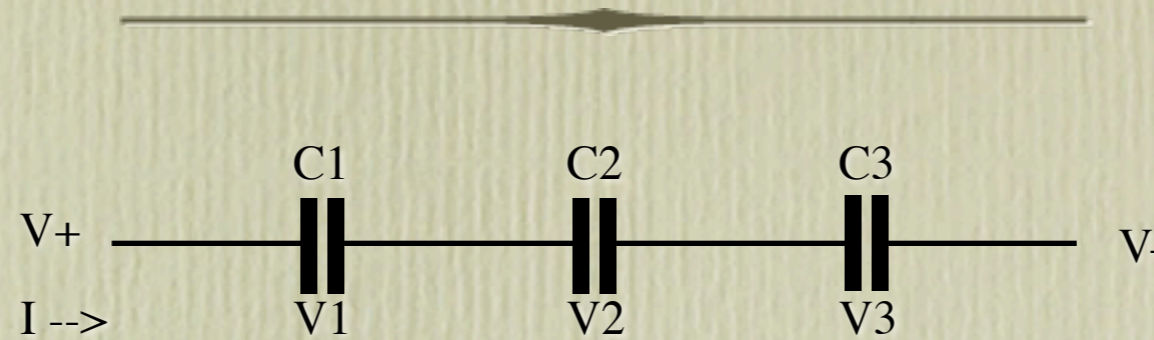

- $C_t = 1 / (1/C_1 + 1/C_2 + \dots)$
- For two capacitors,  $C_t = (C_1 * C_2) / (C_1 + C_2)$
- Always **SMALLER** than the smallest value
- AC Current is the same through all capacitors
- Voltage across each capacitor is dependent on the individual capacitor values

## Parallel:

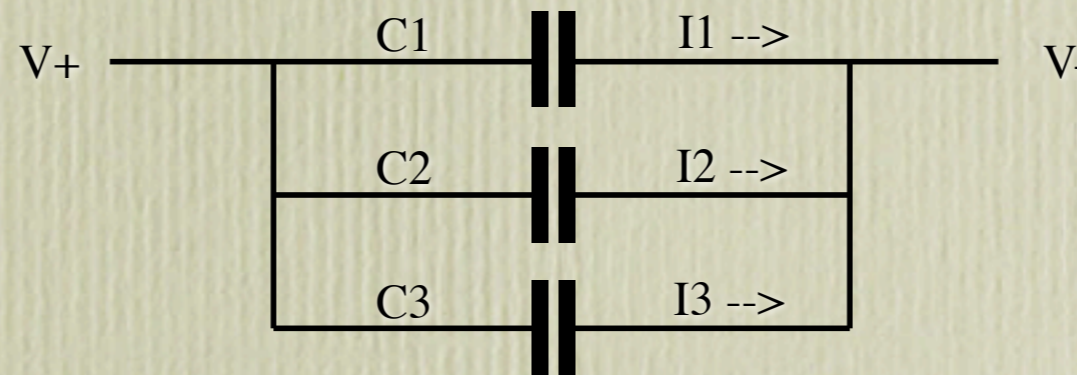

- $C_t = C_1 + C_2 + \dots$
- Always **LARGER** than the largest value
- Voltage is the same across all capacitors
- AC Current through each capacitor is dependent on the individual capacitor values


# Capacitor construction

**Capacitance:  $C \propto \epsilon A/d$**

$\epsilon$ : Permittivity (Dielectric constant)



A: Area of the electrodes

d: Distance between the electrodes

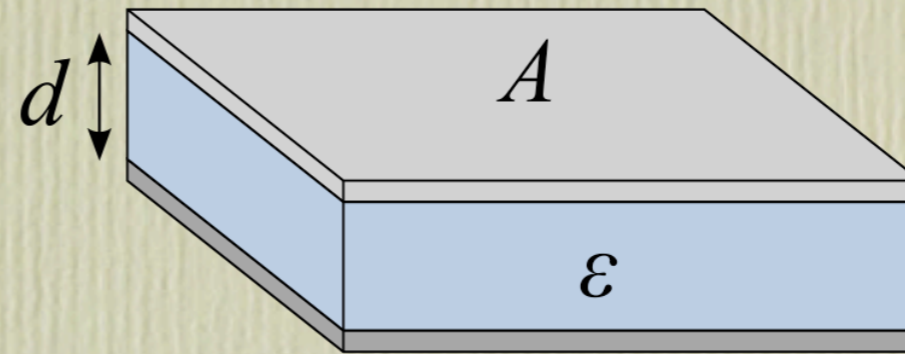

Series

Parallel

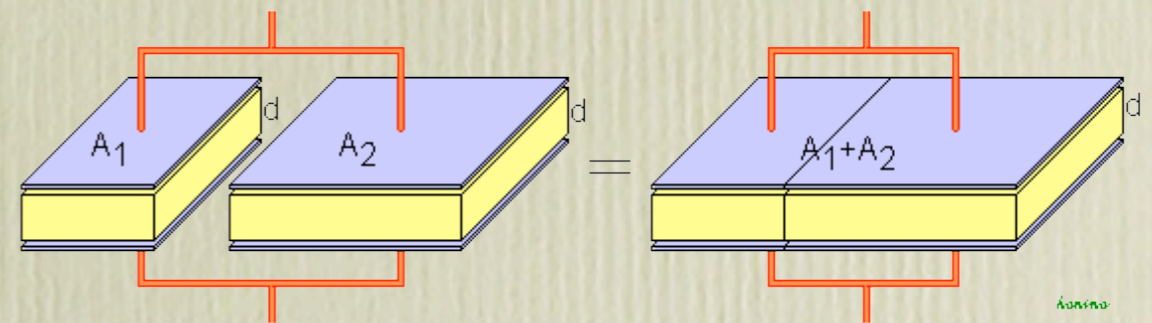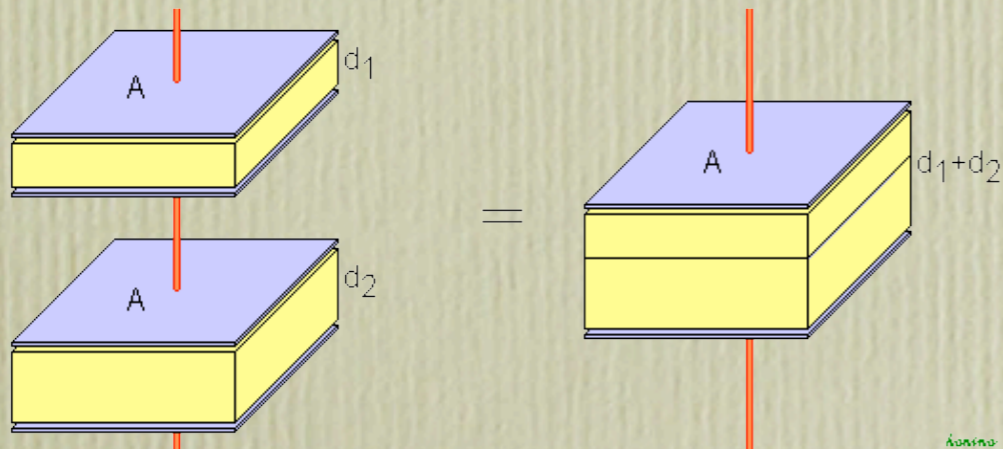

# Test Questions

---

G5C09: What is the capacitance of three  $100\ \mu\text{F}$  capacitors connected in series?

- A)  $0.30\ \mu\text{F}$
- B)  $0.33\ \mu\text{F}$
- C)  $33.3\ \mu\text{F}$
- D)  ~~$300\ \mu\text{F}$~~

•  $C = C_t/3 = 100\ \mu\text{F} / 3 = 33.3\ \mu\text{F}$  (C)

G5C08: What is the equivalent capacitance of two  $5.0\ \text{nF}$  capacitors and one  $750\ \text{pF}$  capacitor connected in parallel?


- A)  $576.9\ \text{nF}$
- B)  ~~$1733\ \text{pF}$~~
- C)  ~~$3583\ \text{pF}$~~
- D)  $10.750\ \text{nF}$

•  $C_t = C_1 + C_2 + C_3 = 5.0 + 5.0 + 0.75 = 10.75\ \text{nF}$  (D)

# Uses

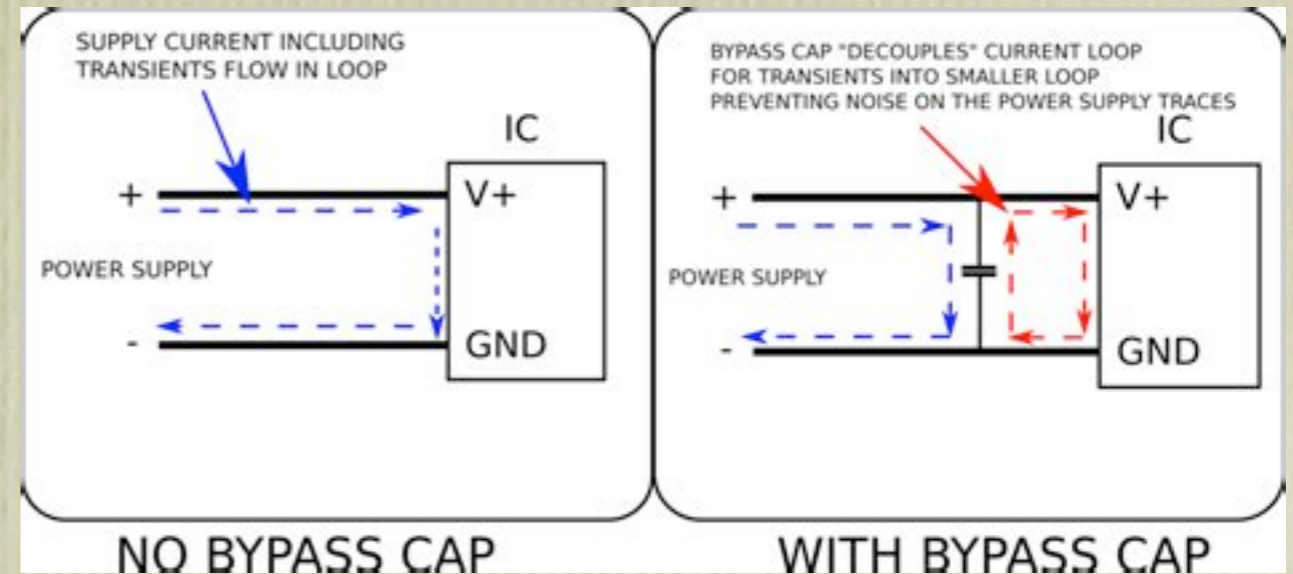
## ► Decoupling / Bypass

Keep high frequency noise from affecting power supply lines


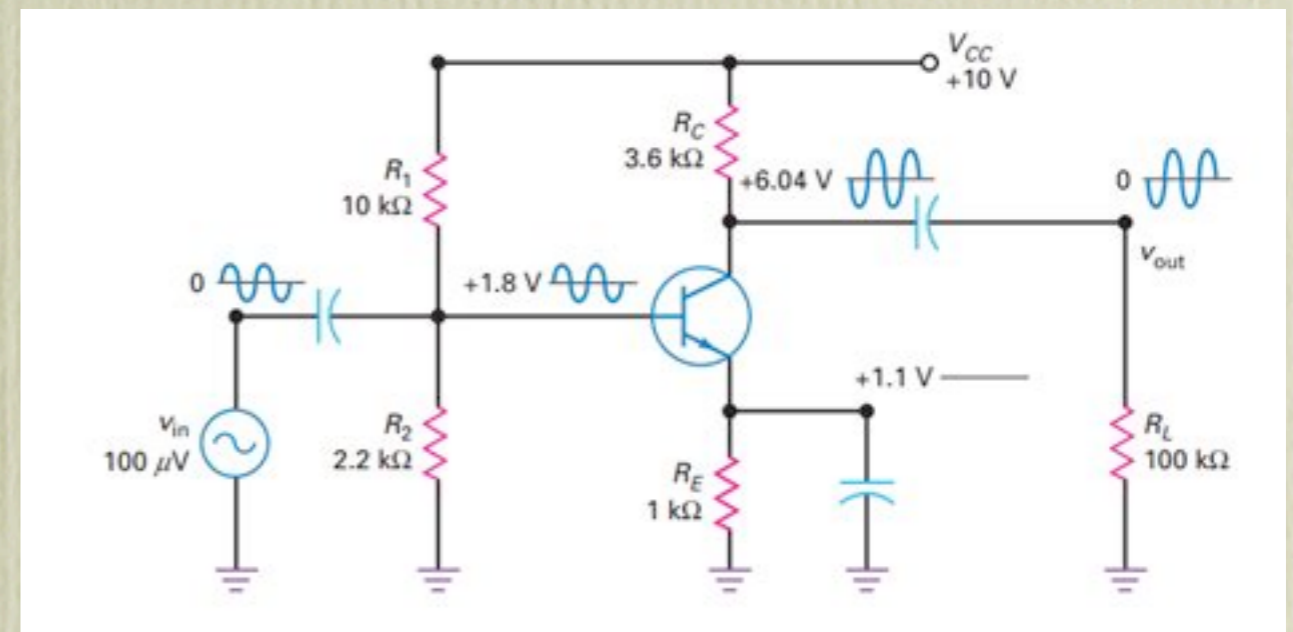
## ► Coupling


Pass AC signals between circuits with different DC voltages



# Uses

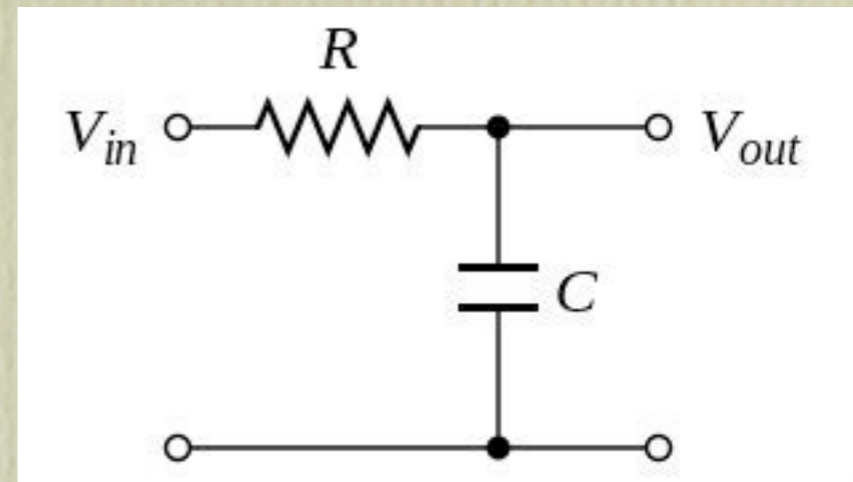
## ► Filtering

Simple (first order) low pass and high pass RC filters



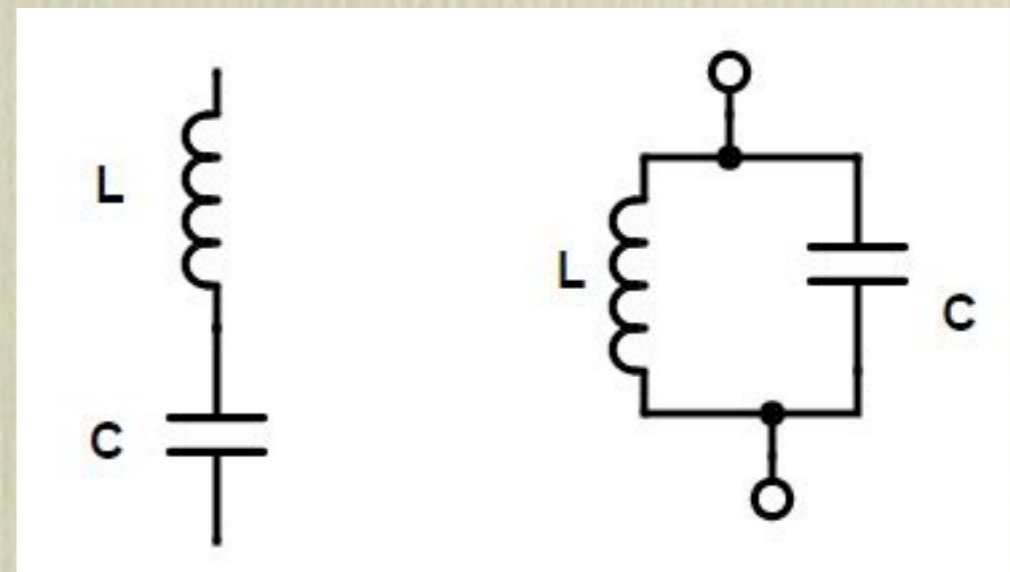
## ► Tuned Circuits

Frequency selectivity when used with an inductor



# Impedance Plot

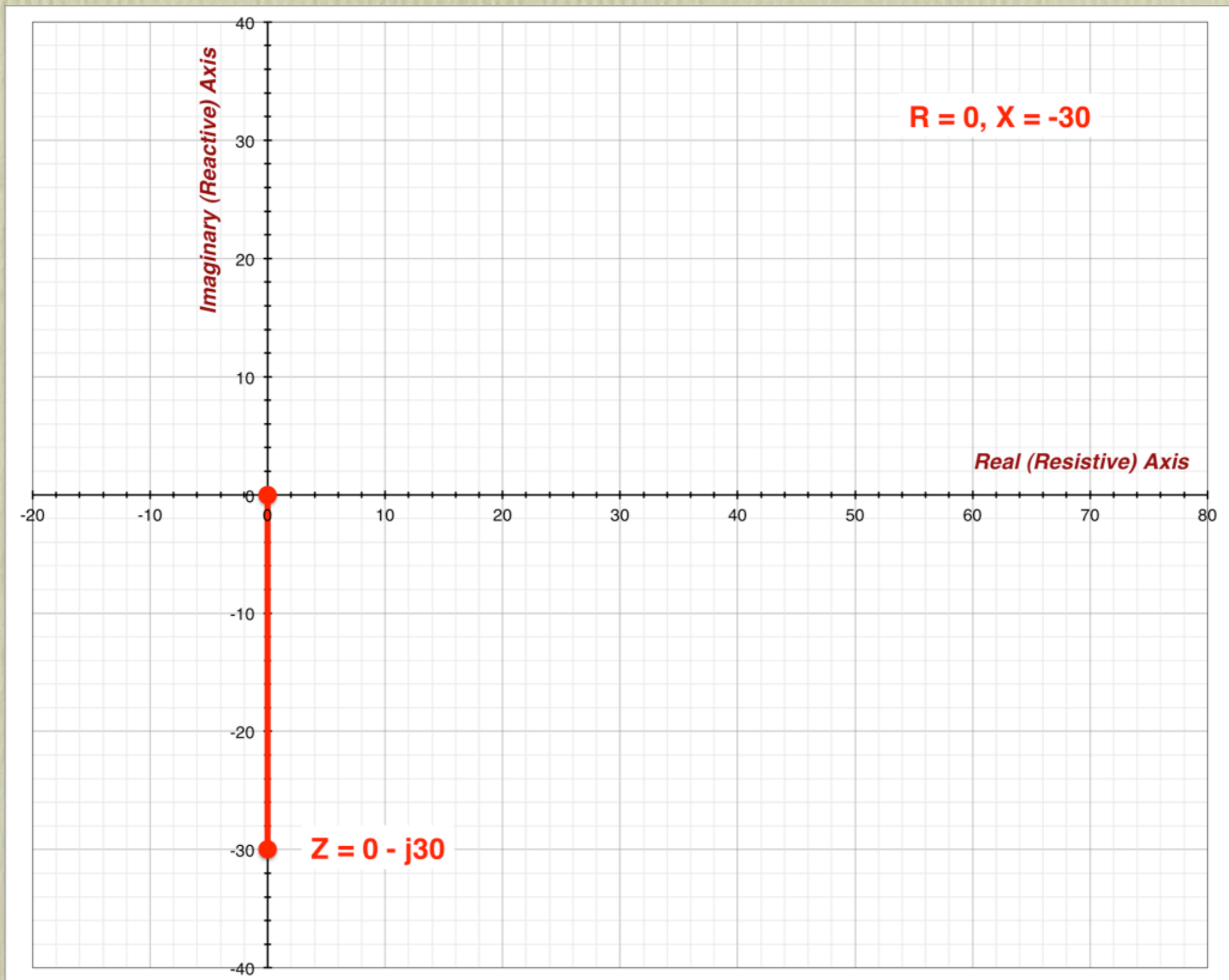

# Inductor




## Characteristics:

- Resists a CHANGE in current
- Stores energy in a magnetic field
  - Ideally any input energy is returned to the source
- Non-polarized
- Cores: Air, Iron, Ferrite (Permeability  $\mu$ )
- Variable: Tapped (Roller inductor), Moveable core
- Usually from nH to H
- Passes DC, Impedes AC
- Voltage across the inductor leads the current by  $90^\circ$  -- ELI the ICE man
- Inductive reactance has a positive phase angle ( $+jX$ )

## Formulas:

- $X_L = 2\pi fL$ ; Reactance increases with an increase in frequency or inductance
- $L = N^2 * AL$ ; Inductance depends on number of turns and Inductance Index
- $V = L di/dt$ 
  - Voltage = Inductance \* Change in current with respect to time

# Inductor

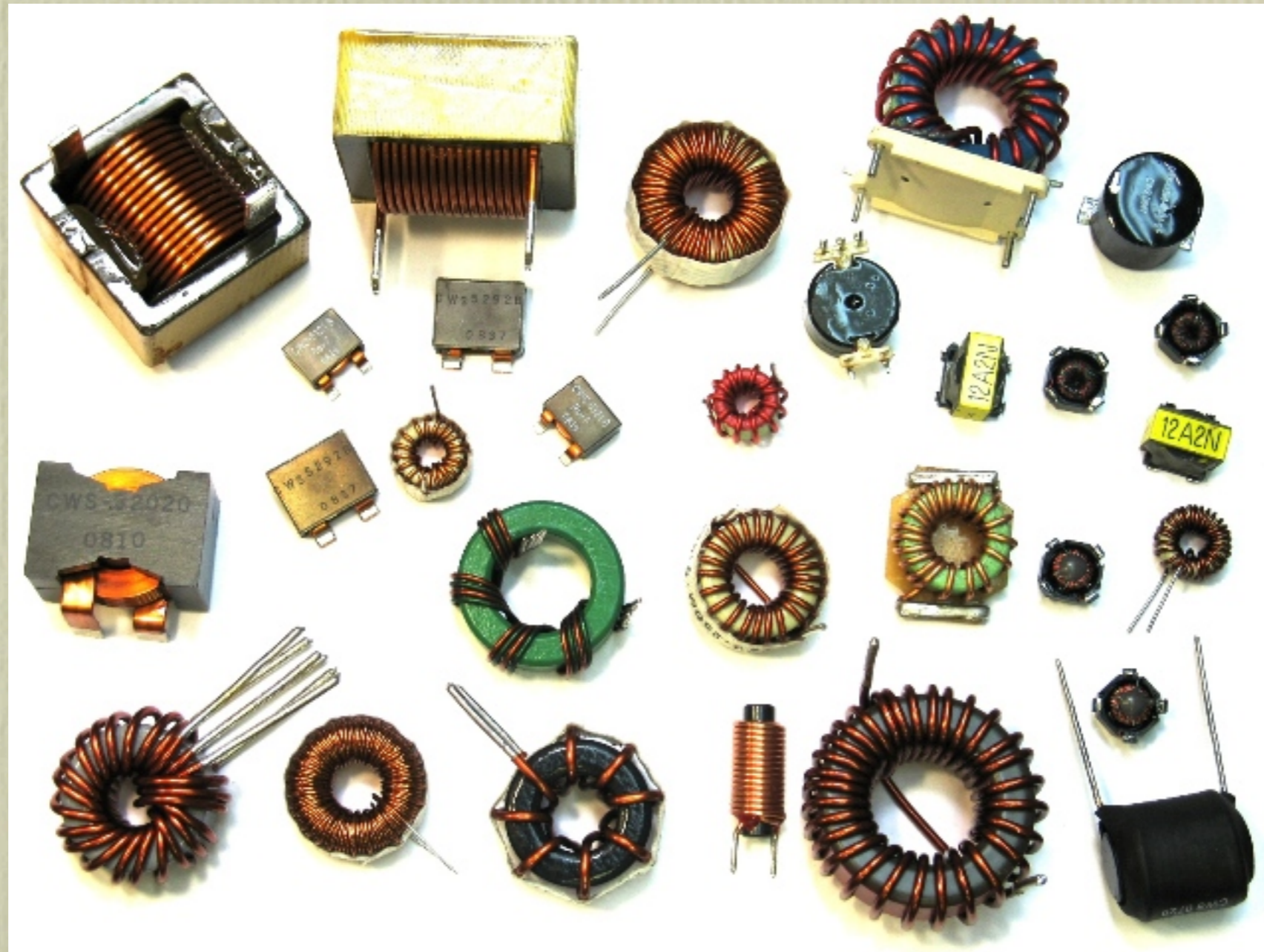



# Test Questions

---

E5D09: What happens to reactive power in an AC circuit that has both ideal inductors and ideal capacitors?

A) It is dissipated as heat in the circuit

**B) It is repeatedly exchanged between the associated magnetic and electric fields, but is not dissipated**

C) It is dissipated as kinetic energy in the circuit

D) It is dissipated in the formation of inductive and capacitive fields

# Test Questions

---

E6D05: What is one reason for using ferrite cores rather than powdered iron in an inductor? **(C)**

- A) Ferrite toroids generally have lower initial permeability
- B) Ferrite toroids generally have better temperature stability
- C) Ferrite toroids generally require fewer turns to produce a given inductance value
- D) Ferrite toroids are easier to use with surface mount technology

E6D06: What core material property determines the inductance of an inductor? **(D)**


- A) Thermal impedance
- B) Resistance
- C) Reactivity
- D) Permeability

E6D08: What is one reason for using powdered-iron cores rather than ferrite cores in an inductor? **(B)**

- A) Powdered-iron cores generally have greater initial permeability
- B) Powdered-iron cores generally maintain their characteristics at higher currents
- C) Powdered-iron cores generally require fewer turns to produce a given inductance
- D) Powdered-iron cores use smaller diameter wire for the same inductance


# Series / Parallel Inductors

## Series:

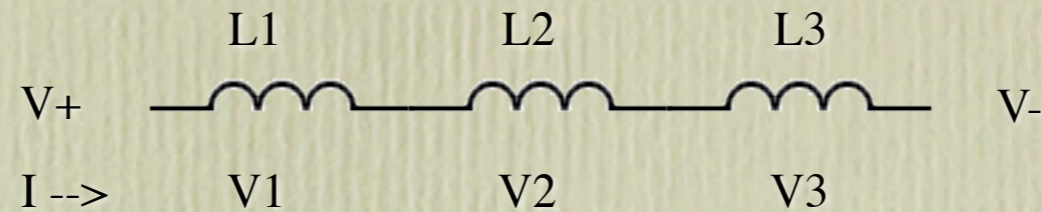

- $L_t = L_1 + L_2 + \dots$
- Always LARGER than the largest value
- Current is the same through all inductors
- Voltage across each inductor is dependent on the individual inductor values

## Parallel:

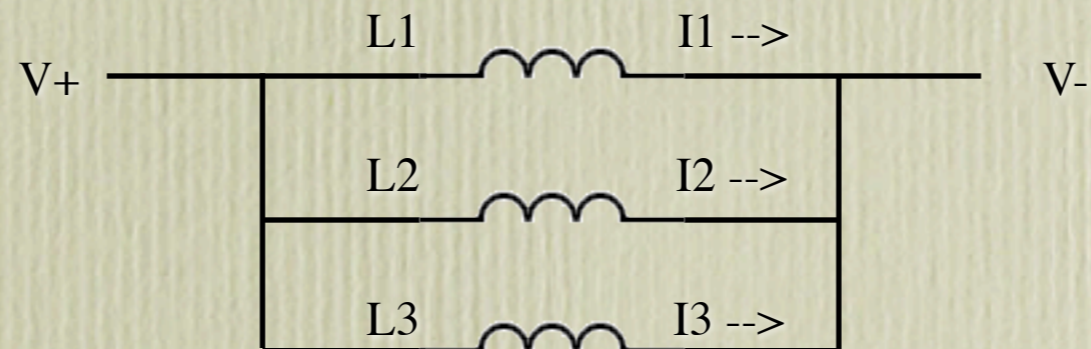

- $L_t = 1 / (1/L_1 + 1/L_2 + \dots)$
- Always SMALLER than the smallest value
- For two inductors,  $L_t = (L_1 * L_2) / (L_1 + L_2)$
- Voltage is the same across all inductors
- Current through each inductor is dependent on the individual inductor values

# Test Questions

---

G5C10: What is the inductance of three 10 mH inductors connected in parallel?

~~A) 0.30 H~~

~~B) 3.3 H~~

C) 3.3 mH

~~D) 30 mH~~

•  $L_{t1} = (L1 * L2) / (L1 + L2) \rightarrow L_{t1} = (10 * 10) / (10 + 10) = 100 / 20 = 5 \text{ mH}$

$L_t = (L_{t1} * L3) / (L_{t1} + L3) = (10 * 5) / (10 + 5) = 50 / 15 = 3.33 \text{ mH (C)}$

- OR -

•  $L_t = 1 / (1/L1 + 1/L2 + 1/L3) = 1 / (1/10 + 1/10 + 1/10) = 1 / (3/10) = 10 / 3 = 3.33 \text{ mH (C)}$

- OR -

•  $L_t = 10 / 3 = 3.33 \text{ mH (C)}$

G5C11: What is the inductance of a 20 mH inductor connected in series with a 50 mH inductor?

~~A) 0.07 mH~~

~~B) 14.3 mH~~

C) 70 mH


~~D) 1000 mH~~

•  $L_t = L1 + L2 = 20 + 50 = 70 \text{ mH (C)}$

# Uses

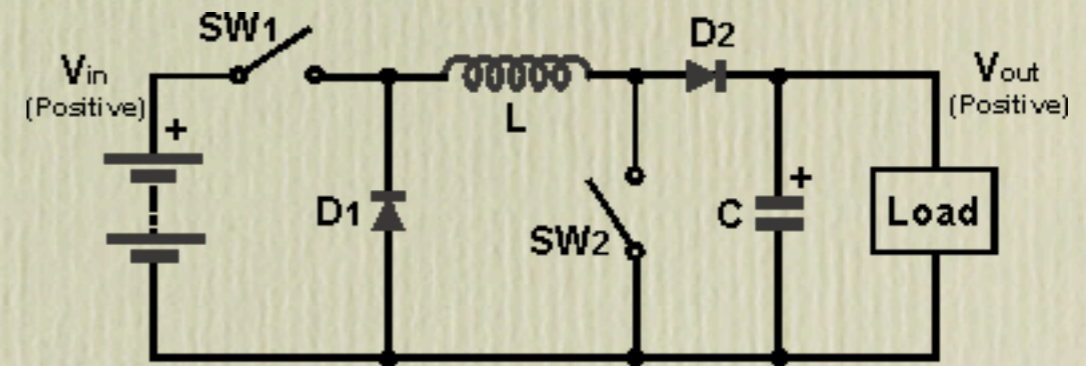
## ► Switching Power Supplies

Energy is stored in the inductor's magnetic field


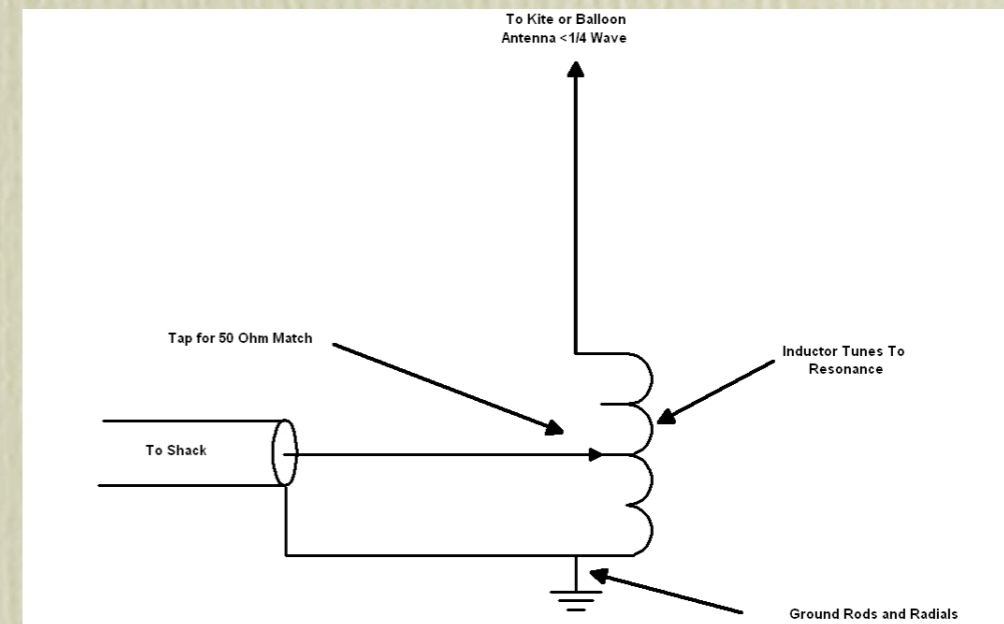
## ► Loading Coil

Tunes out the capacitive reactance of the antenna




# Uses

## ▶ Common Mode Choke

Lots of info from K9YC  
and GM3SEK


X

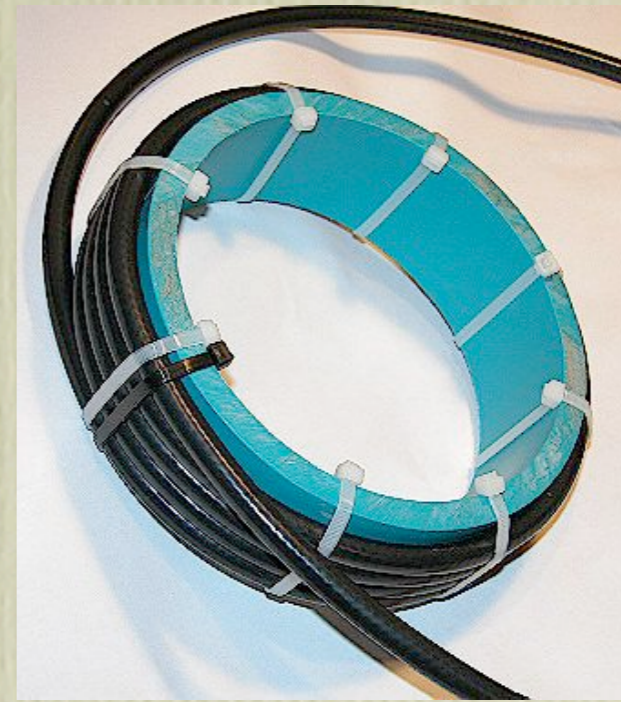

✓



# Impedance Plot

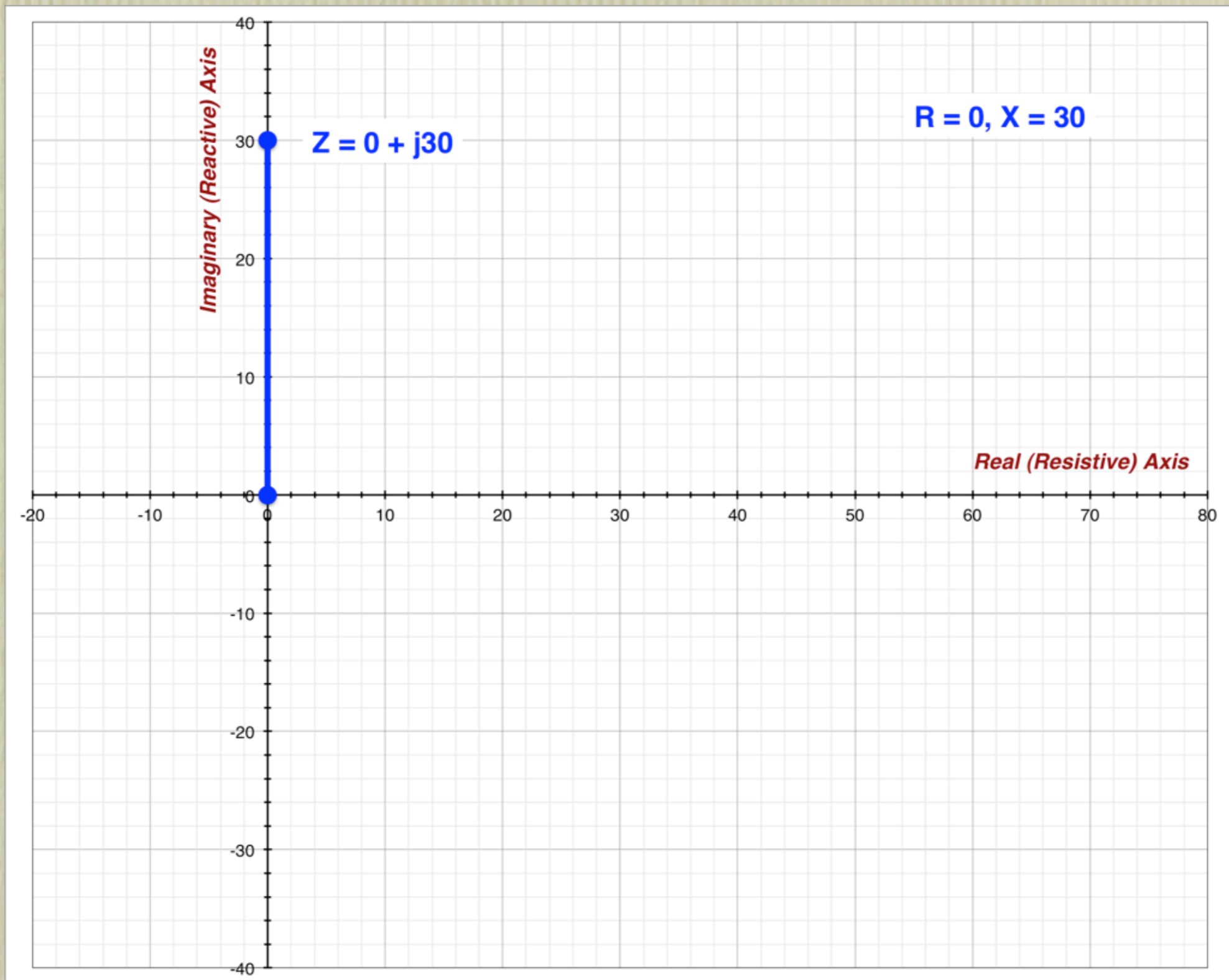

# Transformer

---

## Characteristics:

- Consists of two (or more) coupled inductors - One primary, one or more secondaries
- Only responds to a differential AC input voltage
- Non-polarized (sort of) ...
- Typical Cores: Iron, Ferrite

## Uses:

- Transforming impedance or voltage / current
- Changing a balanced line to an unbalanced line (balun)
- Common mode noise rejection
- Isolation


## Formulas:

If  $N_1$  = Number of turns on the primary,  $N_2$  = Number of turns on the secondary

- Voltage ratio =  $N_2 / N_1$  --->  $V_{Out} = V_{In} * (N_2 / N_1)$
- Current ratio =  $N_1 / N_2$  --->  $I_{Out} = I_{In} * (N_1 / N_2)$ ; **Power must remain constant!**
- Impedance ratio =  $V / I = (N_2 / N_1) / (N_1 / N_2) = (N_2 / N_1)^2$   
-->  $Z_2 = Z_1 * (N_2 / N_1)^2$



# Transformer

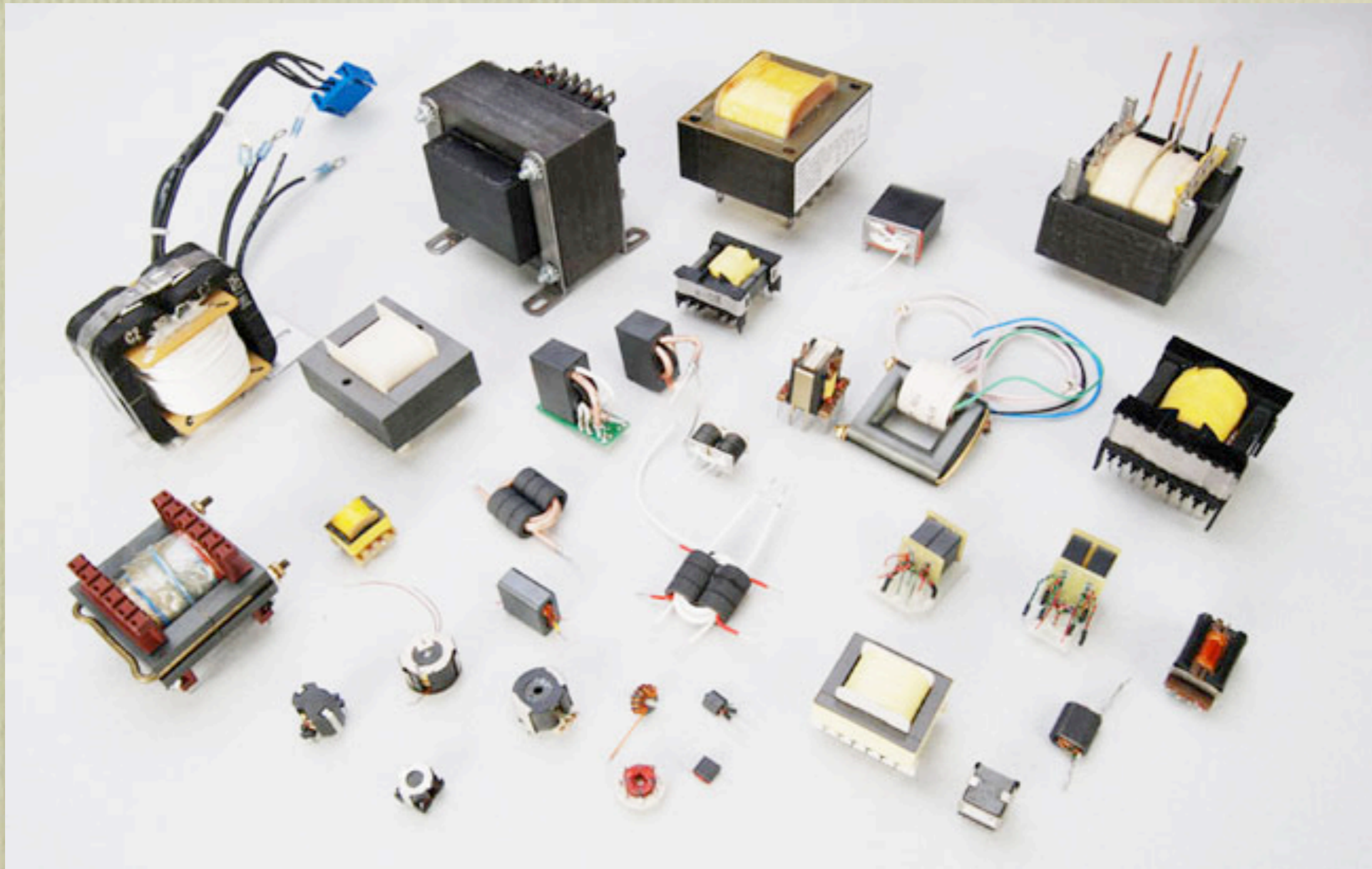

# Test Questions

---

G5C06: What is the RMS voltage across a 500-turn secondary winding in a transformer if the 2250-turn primary is connected to 120 VAC?

- A) ~~2370 volts~~
- B) ~~540 volts~~
- C) 26.7 volts
- D) 5.9 volts

•  $V_{Out} = V_{In} * (N2/N1) = 120 * (500/2250) = 26.7 \text{ Volts (C)}$

G5C07: What is the turns ratio of a transformer used to match an audio amplifier having 600 ohm output impedance to a speaker having 4 ohm impedance?


- A) 12.2 to 1
- B) 24.4 to 1
- C) 150 to 1
- D) 300 to 1

•  $Z2 = Z1 * (N2/N1)^2$ ; By convention Z2 is the highest impedance for turns ratio  
 $(N2/N1) = \text{Sqrt}(Z2/Z1) = \text{Sqrt}(600/4) = \text{Sqrt}(150) = 12.25 \text{ (A)}$

# Uses

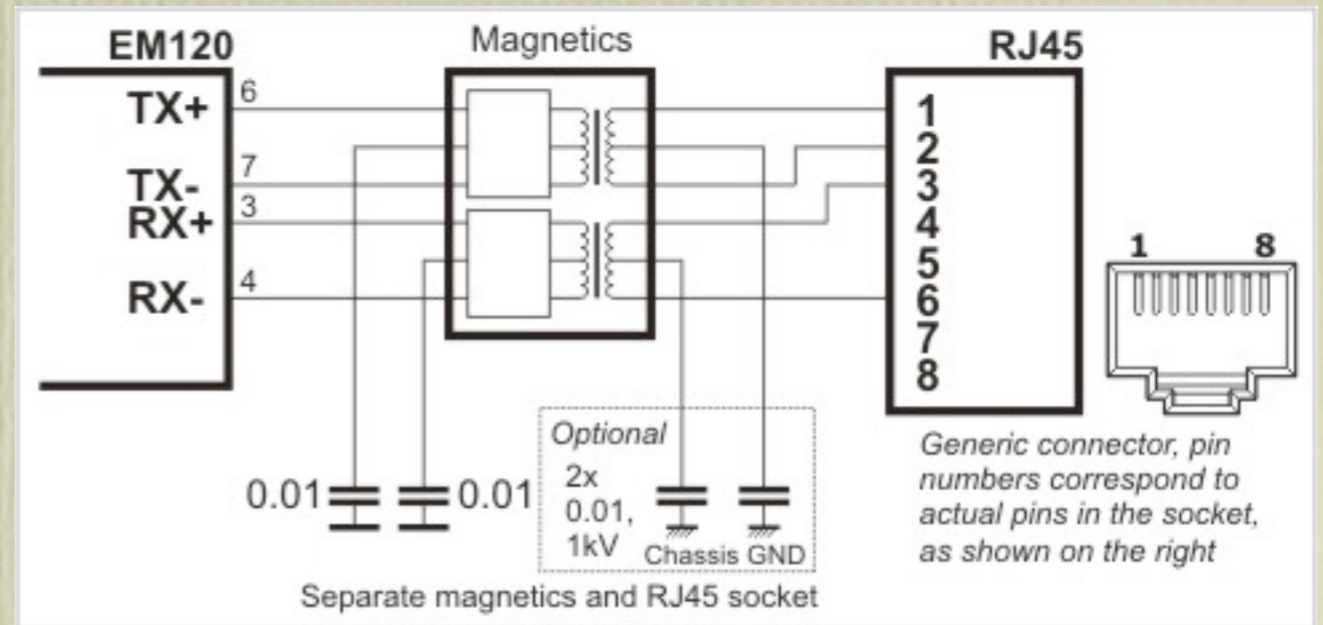
## ► Ethernet

- Eliminate ground loops
- Reject common mode noise


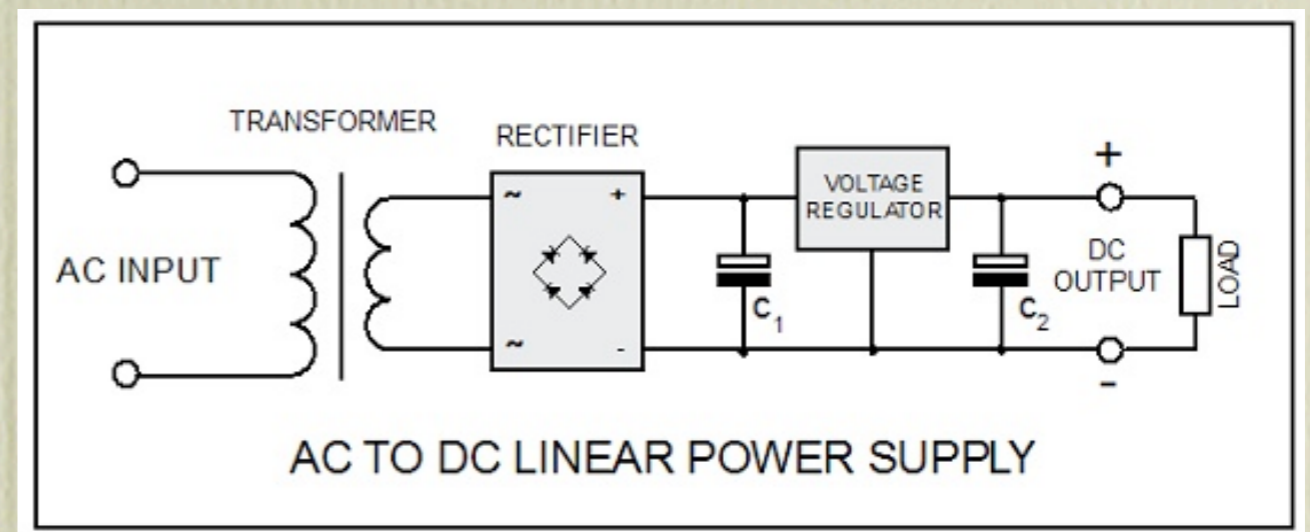
## ► Linear Power Supplies


- Convert line voltage to desired output voltage and current



# Uses

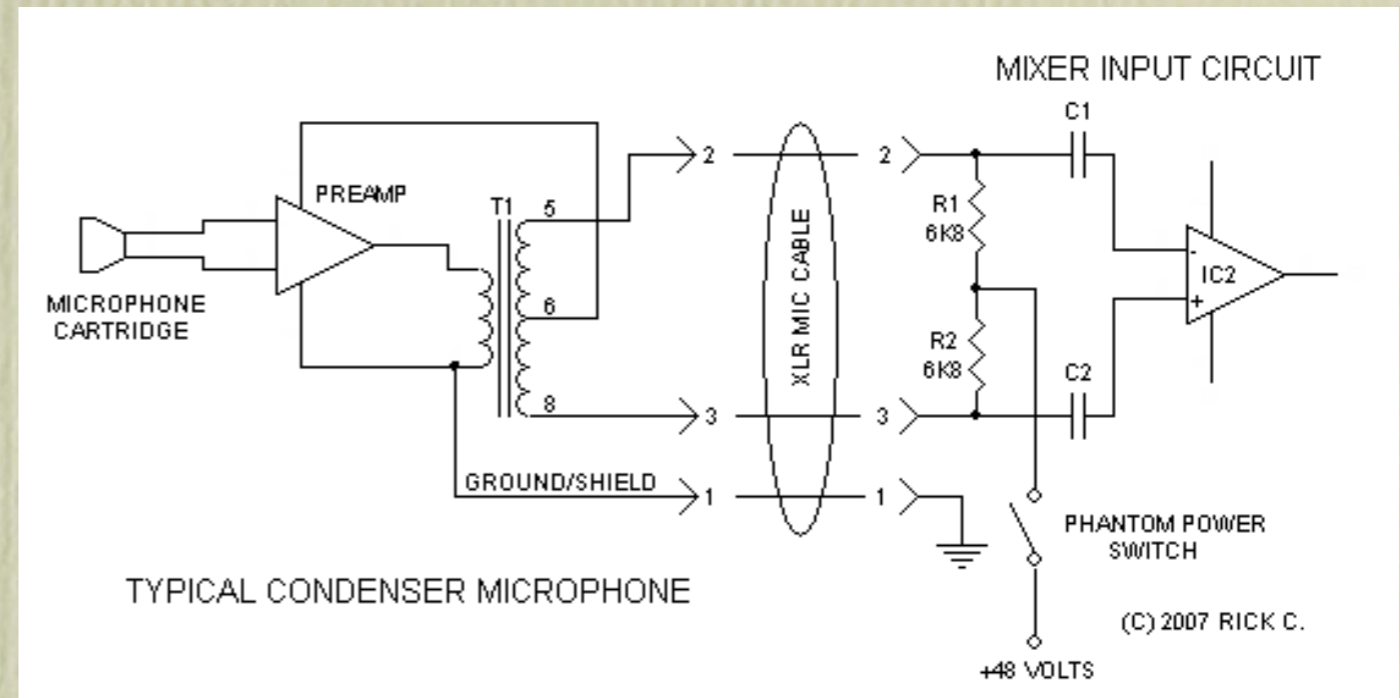
## ► Professional Audio

- Receive phantom power
- Match impedances



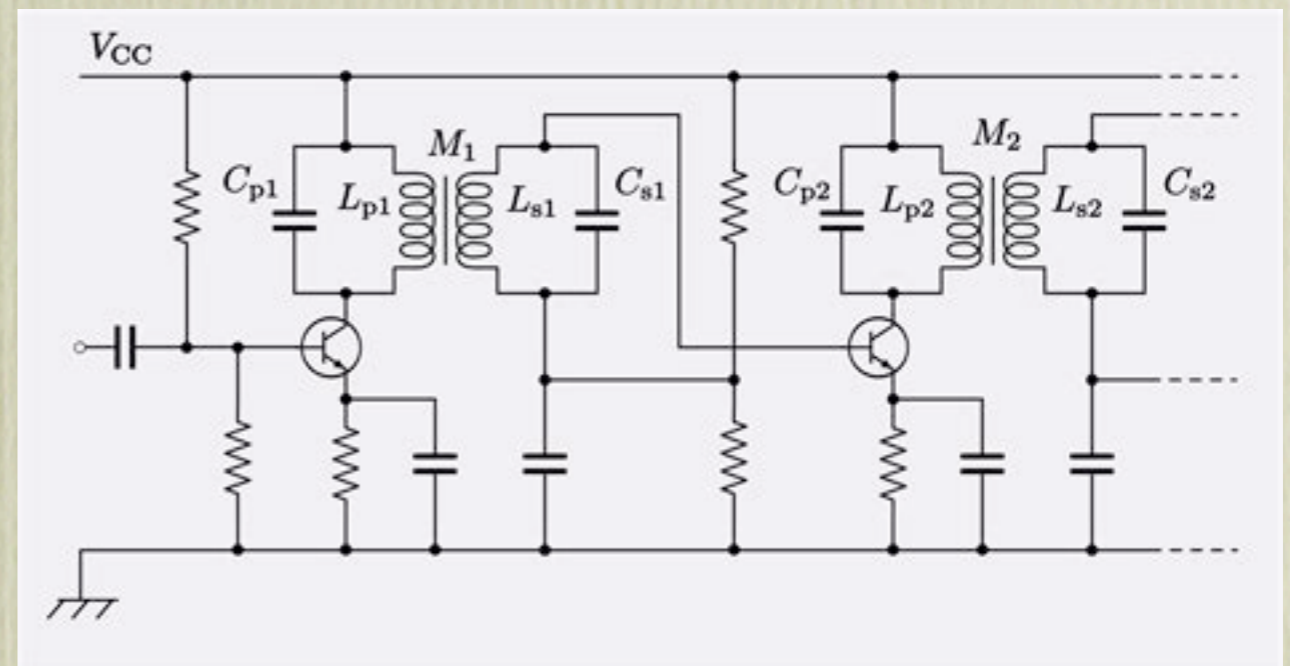
## ► RF Coupling

- Control voltage, impedance and frequency response between stages




# Bias Tee

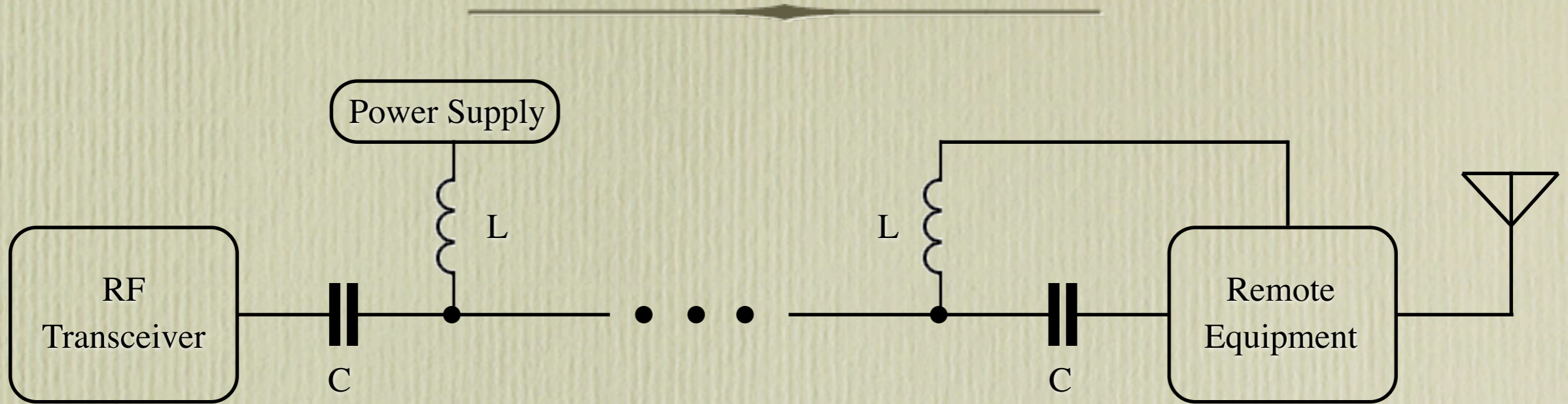



# RLC Demo

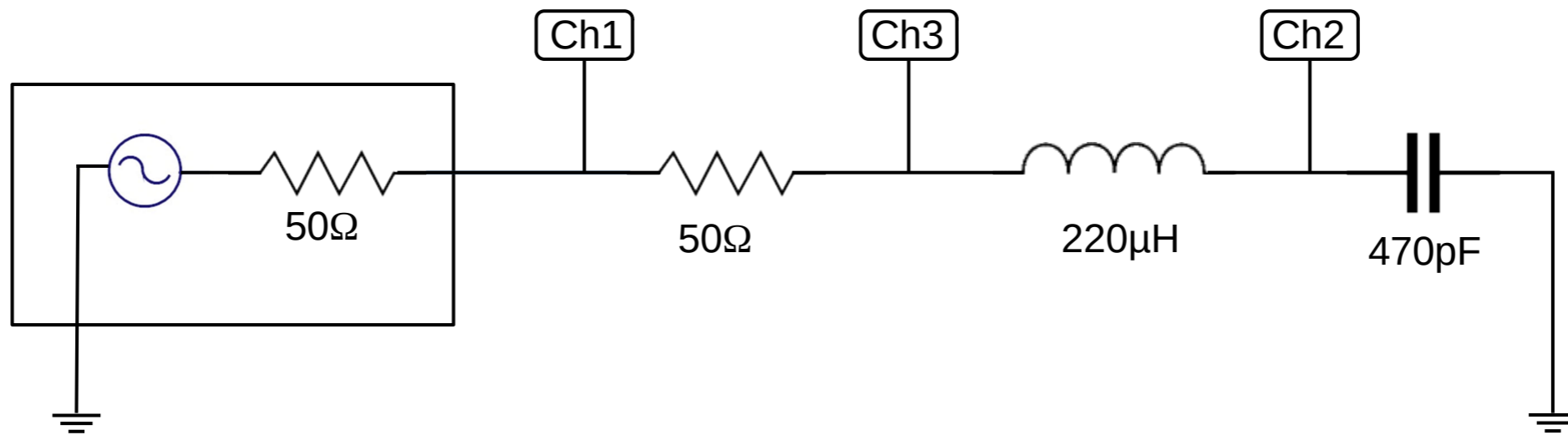

$$X_C = \frac{1}{2\pi fC} \quad X_L = 2\pi fL \quad \text{Resonant if } X_C = X_L \quad \Rightarrow \quad f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi\sqrt{220 \times 10^{-6} \times 470 \times 10^{-12}}} = 494.95 \text{ kHz}$$

$$X_L = 2\pi fL = 2\pi \times 494950 \times 220 \times 10^{-6} = 684 \Omega$$

$$\text{Measure } V_r, \quad I_r = \frac{V_r}{R} = \frac{0.895}{50} = 0.0179 \text{ A}$$

$$V_L = I_r \times X_L = 0.0179 \text{ A} \times 684 \Omega = 12.25 \text{ V}$$

